

Universidade do Vale do Itajaí
Computer Engineering
Basic Electronics

**Final Assignment for Basic
Electronics**

Student: Lucas Mateus Gonçalves
Teacher Advisor: Walter Antonio Gontijo

December
2021

Universidade do Vale do Itajaí
Computer Engineering
Basic Electronics

**Final Assignment for Basic
Electronics**

Final Assignment, including test simulations for Basic Electronics presented for the class of the Tenth of December, 2021.

Student: Lucas Mateus Gonçalves

Teacher Advisor: Walter Antonio Gontijo

December
2021

Contents


1	Objective	1
2	BC Amplifier	2
2.1	DC analysis	2
2.2	AC analysis	3
3	Emitter Polarization Circuit	5
3.1	DC analysis	5
3.2	AC analysis	6
3.3	AC without the capacitor	7
3.4	AC with the capacitor	7
4	Emitter Voltage Divider	7
4.1	DC analysis	9
4.2	AC analysis	10
4.3	Simulation	10

1 Objective

AC Analysis of circuits containing *NPN* and *PNP* transistors and their simulations, along with the final test simulations.

2 BC Amplifier

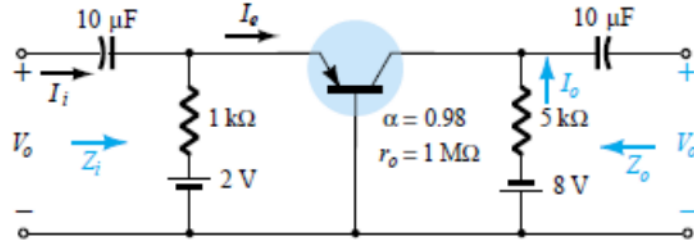This circuit was also seen in the final test.



$$r_e = \frac{26mV}{I_E}$$

2.1 DC analysis

To ensure that the transistor is in an active state, otherwise it would be pointless to perform an *AC* analysis, the *DC* analysis must return the voltages for the transistor's nodes.

The I_E current will simply be the current going the *emitter's* resistor minus the transistor *emitter to base* drop and the extra voltage supply.

$$I_E = \frac{2V - 0.7V}{1k} = 1.3mA$$

Since the hFe is below 100,

$$\beta = \frac{\alpha}{1 - \alpha} = 49$$

The *emitter* current is different from the *collector* current.

$$I_C = \alpha I_E = 98 \times 1.3m = 1.27mA$$

Since we know some of the voltages already,

$$V_B = 0V, V_E = 0.7V$$

the only remaining voltage to confirm the transistor is active is V_C .


$$V_C = -8V + 1.27mA \times 5k\Omega = -1.63V$$

Since V_B and V_E are polarized appropriately but V_B and V_C are reverse, the transistor is active and the *AC* analysis can be performed.

If the transistor was either inactive or saturated however, there would be no output or a constant output respectively.

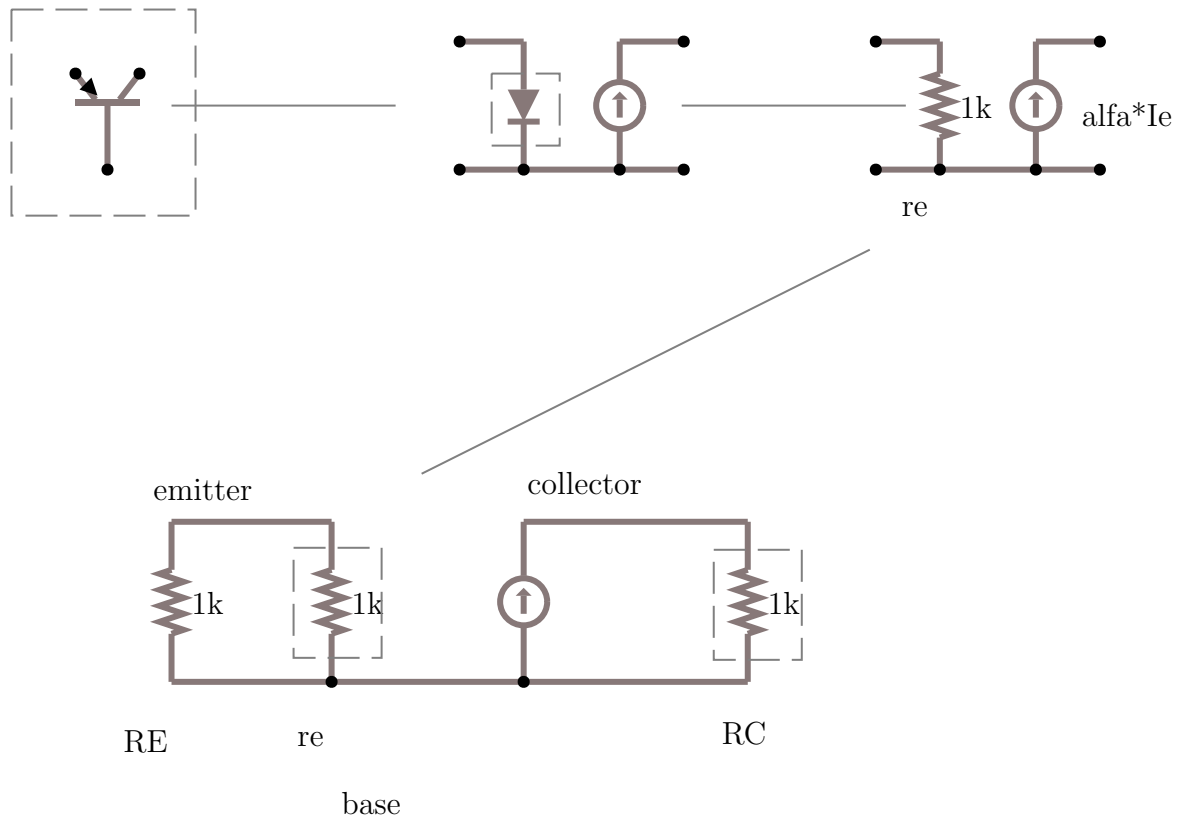2.2 AC analysis

The AC analysis requires a change in the circuit for a simpler one that can be calculated accordingly.



$$A_v(\text{AC gain}) = \alpha R_C / r_e$$

The equations are as such for the impedance's and AC gain of this specific circuit.

$$Z_o(\text{AC output Impedance}) = R_C$$

$$Z_i(\text{AC input Impedance}) = R_E // r_e$$


$$A_v(\text{AC gain}) = \frac{R_C}{r_e}$$

Which when calculated are as follows.

$$Z_o = 5k\Omega$$

$$Z_i = \frac{1k \times 20}{1k + 20} = 19.6\Omega$$

$$A_v = \frac{5k}{20} = 250$$

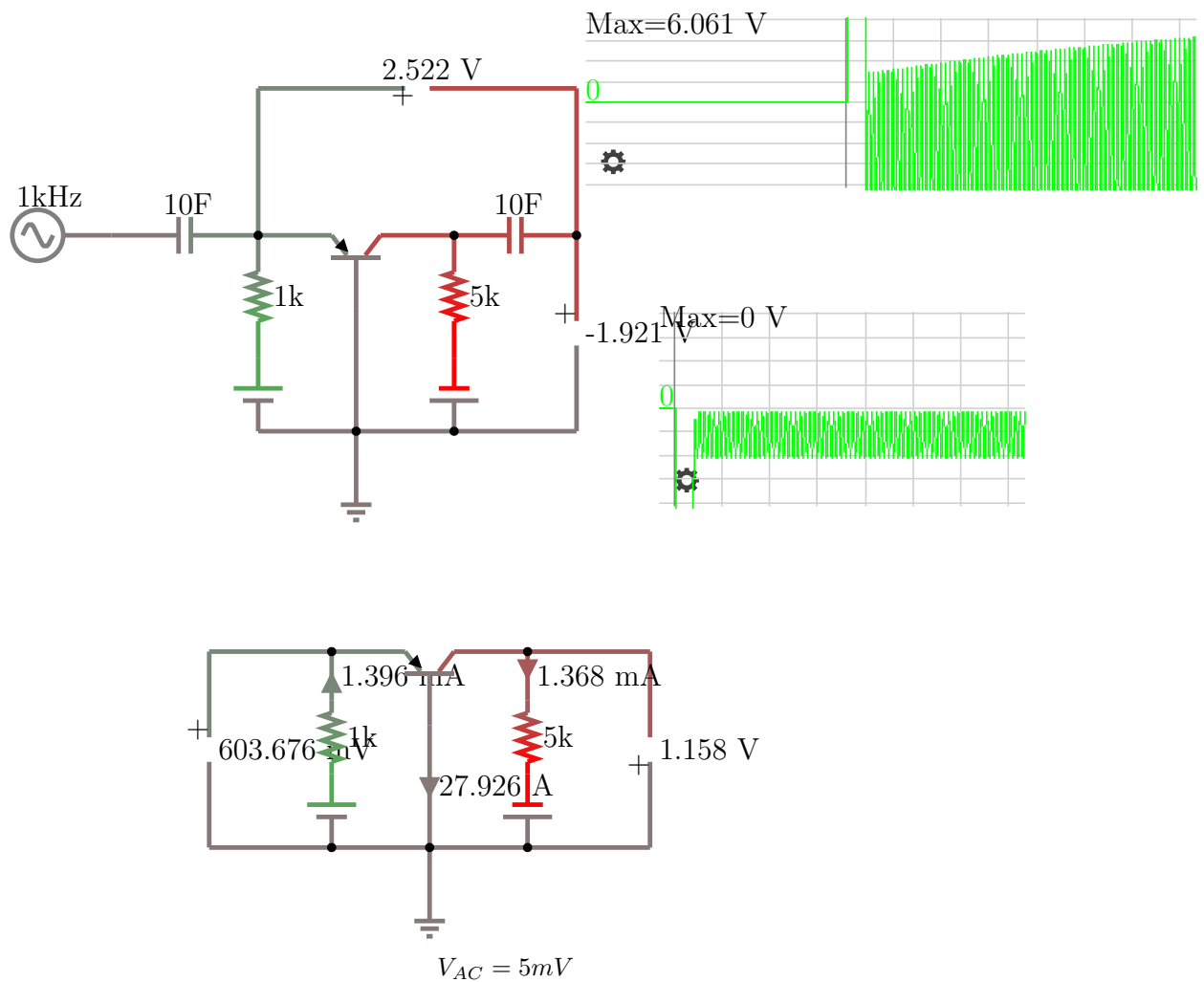


The figure before is the *AC* and *DC* components of the circuits, mind that the simulator takes into account multiple other variables that are not calculated here, which is why the values are a bit skewed.

Mind also that the graphs shown are *AC* coupled, they do have a *DC* component from the supplies.

3 Emitter Polarization Circuit

The following circuit will be analysed.

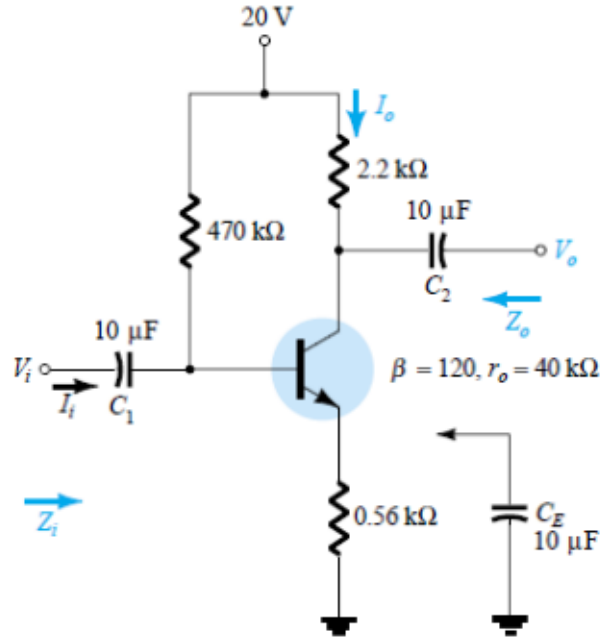

3.1 DC analysis

Since this type of circuit has been analysed before and this paper intends to explain *AC* analysis, the values for the currents and voltages will be show, but not their formulas.

$$I_B = 36\mu A$$

$$I_C = 4.3mA$$

$$I_E = 4.35mA$$

$$V_B = 3V$$

$$V_C = 10.5V$$

$$V_E = 2.45V$$

The *DC* analysis works with C_E attached to the circuit, as a capacitor does not affect a *DC* signal.

3.2 AC analysis

The equations are as follows.

Without the capacitor.

$$Z_i = R_B // Z_b$$

$$Z_b \approx \beta (r_e + R_E)$$

$$Z_o = R_C$$

$$A_v = \frac{\beta R_C}{Z_b}$$

$$r_e = \frac{26}{I_E}$$


With the capacitor, mid the fact that the capacitor nullifies the resistor, being a short circuit in an AC analysis.

$$Z_i = R_B // \beta r_e$$

$$Z_o = R_C$$

$$A_v = -\frac{R_C}{r_e}$$

3.3 AC without the capacitor

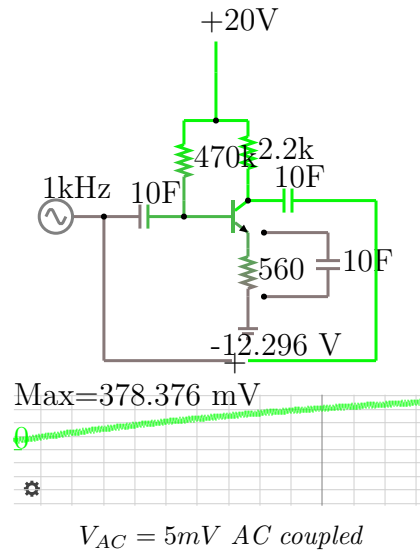

$$r_e = \frac{26}{I_E} = \frac{26}{4.35mA} = 7761.19\Omega$$

$$Z_b \approx \beta (r_e + R_E) = 120 (7761.19 + 560) = 998542.9 \approx 100k\Omega$$

$$Z_i = R_B // Z_b = 82456.14$$


$$Z_o = R_C = 2.2k$$

$$A_v = \frac{\beta R_C}{Z_b} = 2.64$$

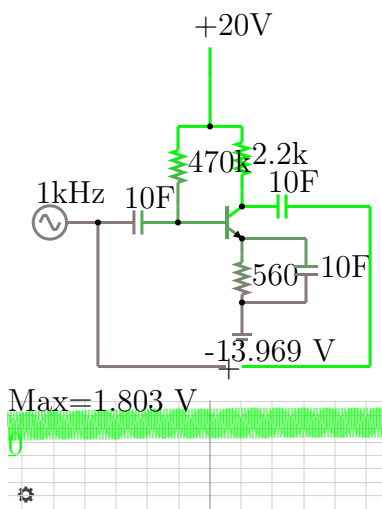3.4 AC with the capacitor

4 Emitter Voltage Divider

The following circuit present in the test is this.



$V_{AC} = 5mV$ AC coupled


$$r_e = \frac{26}{I_E} = \frac{26}{4.35mA} = 7761.19\Omega$$

$$Z_i = R_B // Z_b = 82456.14\Omega$$

$$Z_o = R_C = 2.2k\Omega$$

$$A_v = -\frac{R_C}{r_e} = 0.022$$

10 10mV p-p, frequency 1kHz, gain

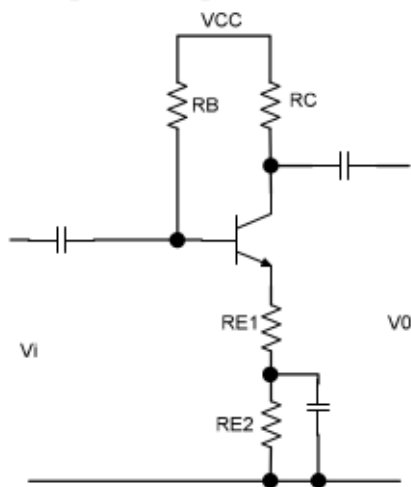

$$V_E = 0.2V_{CC} = 2V$$

$$V_C = 0.5V_{CC} = 5V$$

$$Z_i \geq 10k\Omega$$

$$V_{CC} = 10V$$

$$I_E = 1mA$$

$$\beta = 99$$

4.1 DC analysis

$$V_B = V_E + 0.7V = 2.7V$$

$$R_E = \frac{2V}{1mA} = 2k\Omega$$

$$I_B = \frac{1mA}{99} = 1.01e^{-5}$$

$$R_B = \frac{V_{CC} - V_B}{I_B} = 722.2k\Omega$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = 5k\Omega$$

$$R_{E1} = R_{E2} = 2.5k\Omega$$

4.2 AC analysis

$$r_e = \frac{26}{I_E} = \frac{26}{1mA} = 26k\Omega$$


$$Z_i = R_B // \beta r_e = \frac{722.2k \times 26k}{722.2k + 26k} = 25.1k$$

$$Z_o = R_C = 5k$$


$$Z_b \approx \beta (r_e + R_E) = 3360k\Omega$$

$$A_v = -\frac{\beta R_C}{Z_b} = -0.178$$

4.3 Simulation

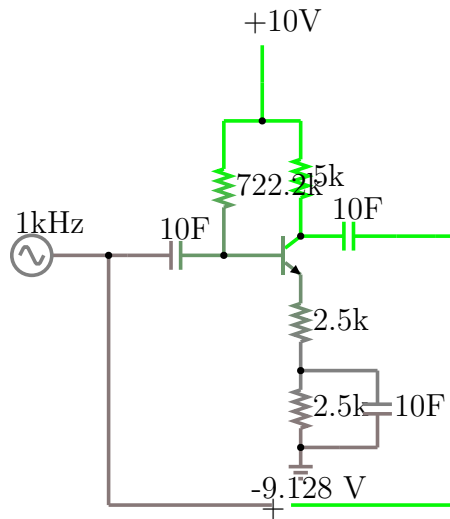

Max=206.883 mV

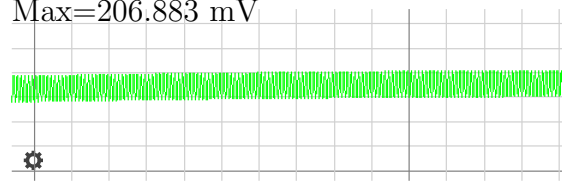

$V_{AC} = 5mV$