

Universidade do Vale do Itajaí
Computer Engineering
Basic Electronics

**Eight Assignment for Basic
Electronics**

Student: Lucas Mateus Gonçalves
Teacher Advisor: Walter Antonio Gontijo

October
2021

Universidade do Vale do Itajaí
Computer Engineering
Basic Electronics

**Eight Assignment for Basic
Electronics**

Eight Assignment for Basic Electronics presented
for the class of the Eight of October, 2021.

Student: Lucas Mateus Gonçalves

Teacher Advisor: Walter Antonio Gontijo

October
2021

Conteúdo

1	Objective	1
2	Introduction	1
3	Simulations	2
3.1	2N3904	2
3.2	2N4124	3
3.3	ZTX1048A	3
4	Extracting useful data from graphs	3

1 Objective

The analysis of multiple *NPN* transistors and their operation regions.

2 Introduction

This paper will describe the *Characteristic Curve*, or operation regions of multiple transistors based on the following circuit.

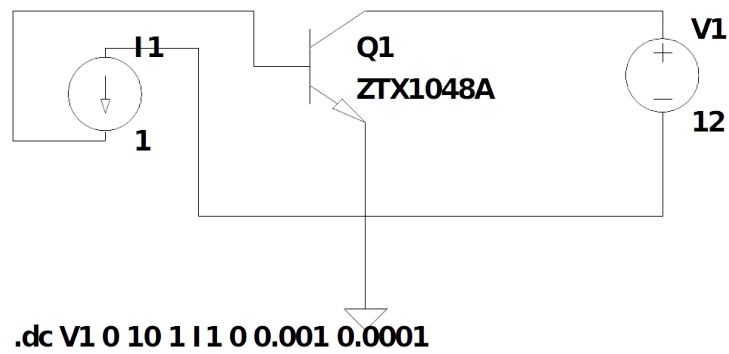


Figura 1: The following circuit shows the ZTX1048A transistor, but multiple will be tested. The simulation parameters are: V1[0V-10V], I1[0A-0.001A].

3 Simulations

The simulator *LTSpice XVII* was used to test the following transistors.

- 2N3904, from *NPX* manufacturer, $I_c[mA] = 200$
- 2N4124, from *Fairchild* manufacturer, $I_c[mA] = 200$
- ZTX1048A, from *Zetex* manufacturer, $I_c[mA] = 5000$

3.1 2N3904

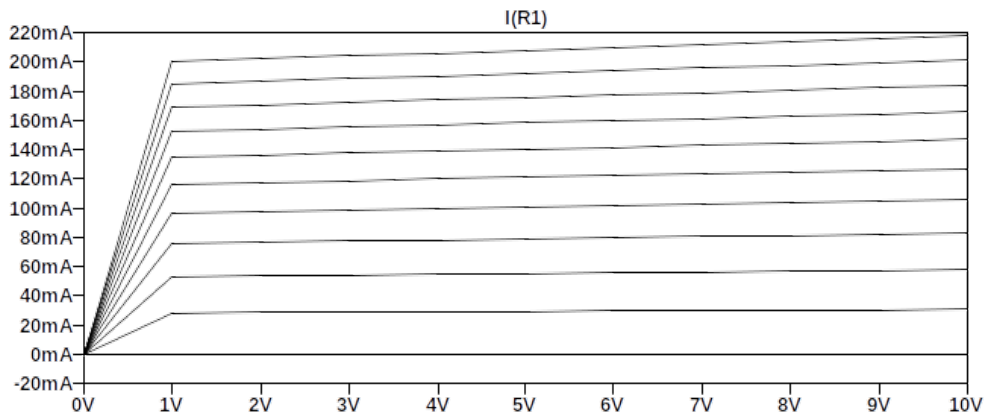


Figura 2: Collector Current ($I_c = 200mA$, Collector Emmitter Voltage (V_{ce}) = 40V at 25°C.

3.2 2N4124

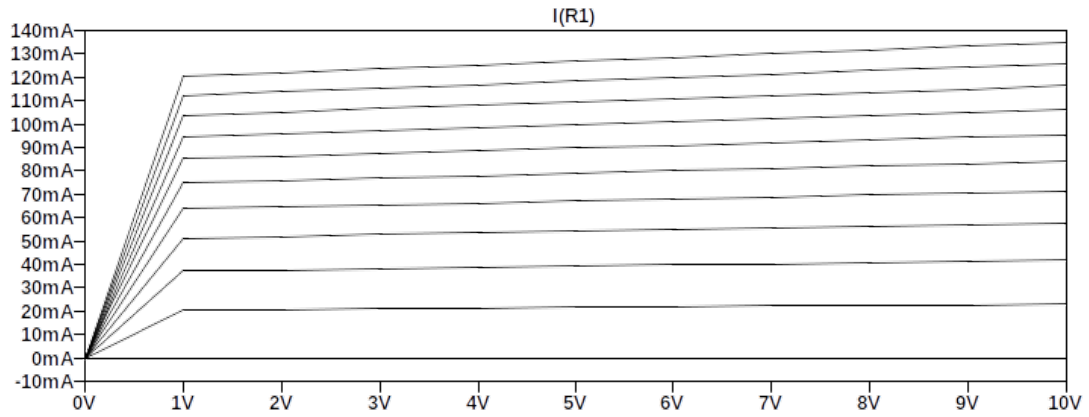


Figura 3: Collector Current (I_c) = 200mA, Collector Emmitter Voltage (V_{ce}) = 25V at 25°C.

3.3 ZTX1048A

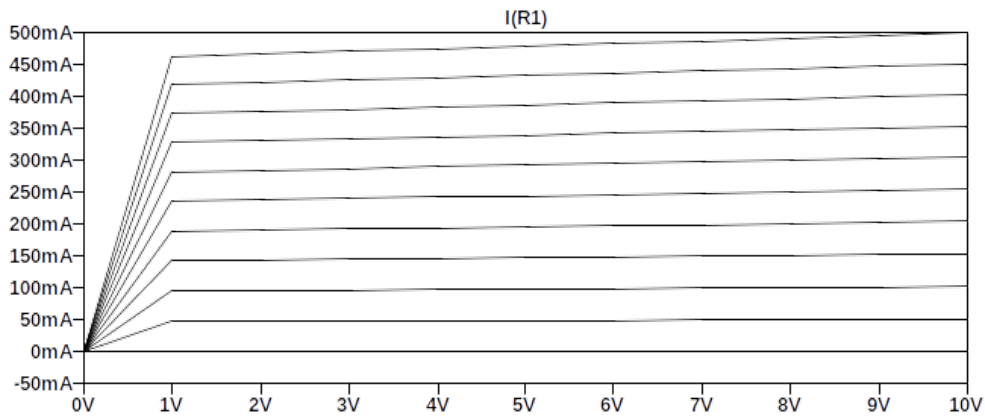


Figura 4: Collector Current (I_c) = 5000mA, Collector Emmitter Voltage (V_{ce}) = 17V at 25°C.

4 Extracting useful data from graphs

The transistor under analysis will be the *Fairchild's* 2N4124.

The graph shows the current through the collector through to the emitter. It is not shown, but every line refers to a base to emitter current of $0.11mA$ from $0.0A$.

Taking the top most line, where the base to emitter current is $1mA$, and at $10V$ collector to emitter voltage, the α and β can be calculated as.

$$\beta = \frac{I_C}{I_B} = \frac{130mA}{1mA} = 130$$

Do note that neither α or β have units, they are ratios.

$$\alpha = \frac{\beta}{\beta + 1} = \frac{130}{130 + 1} = 0.9924$$

The same equations can be used in every point in the *active, or linear* regions.